



DIGITAL DESIGN USING VERILOG

LAB MANUAL

18ECL47



SEMESTER: IV**DSD USING VERILOG LAB**

Course Code	18ECL47	Credits	01
Hours/Week(L-T-P)	0-0-2	CIE Marks	50
Total Hours	26(P)	SEE Marks	50
Exam Hours	03	Course Type	Core Lab

PRE-REQUISITES

- Digital Electronics

COURSE OUTCOMES

1. Familiarize with EDA tools for simulation, verification and synthesis of digital design.
2. Simulate Combinational circuits in Dataflow, Behavioral and Gate level Abstraction using Verilog HDL code
3. Program sequential circuits like flip flops and counters in Behavioral description and obtain simulation waveforms.
4. Implement Combinational and Sequential circuits on FPGA and test the hardware.
5. Interface/Emulate the hardware to the FPGA and obtain the required output

LIST OF EXPERIMENTS

1. Realization of logic gates using Verilog HDL code and three/ four variable expression
2. Realization of combinational designs using Verilog HDL code
 - a. 2 to 4 decoders
 - b. 8 to 3 (encoder without priority & with priority)
 - c. 8 to 1 multiplexer
 - d. 1 to 8 De Multiplexer
 - e. 4 bit binary to gray converter and vice versa
 - f. Comparator.
3. Realize and verify the function of a Full Adder in three modelling styles using HDL code .
4. Realization of N- bit ALU for the give function
5. Develop the HDL Code for the following flip-flops: SR, D, JK, and T
6. Design BCD counters (Synchronous reset and asynchronous reset) and “any sequence” counters.

Note: Test bench program should be written for all the above experiments

CO-PO-PSO MAPPING

CO/ PO	PO 1	PO 2	PO 3	PO 4	PO 5	PO 6	PO 7	PO 8	PO 9	PO 10	PO 11	PO 12	PSO 1	PSO 2	PSO 3	BT
CO1	3		1		2				2	2		3	3			2
CO2	3	2	2		2				2	2		3	3		1	3
CO3	3	2	2		2				2	2		3	3		1	3
CO4	3	3	2	2	2				2	2		3	3	1	1	3
CO5	3	3	2	2	2				2	2		3	3	1	1	3

Experiment 1

Aim : Realization of logic gates using Verilog HDL code in all three modelling style .

Gate Level Modelling

```
module LogicGates(a,b,y);  
input a,b;  
output [0:6]y;  
not(y[0],a);  
and(y[1], a,b);  
or(y[2],a,b);  
nand(y[3],a,b);  
nor(y[4],a,b);  
xor(y[5],a,b);  
xnor(y[6],a,b);  
endmodule
```

Behavioral Modelling

```
module gates (a, b, y);  
input a, b;  
output reg [0:6]y;  
  
always @ (a or b)  
begin  
y[0]=~a;  
y[1]=a&b;  
y[2]=a|b;  
y[3]=~(a &b);  
y[4]=~(a|b);  
y[5]=a^b;  
y[6]=~(a^b);  
end  
endmodule
```

Data flow modelling

```
module gates (a, b, y);  
input a, b;  
output [0:6]y;  
  
assign y[0]=~a;
```

```
assign y[1]=a&b;
assign y[2]=a|b;
assign y[3]=~(a &b);
assign y[4]=~(a|b);
assign y[5]=a^b;
assign y[6]=~(a^b);
end
endmodule
```

Test bench

```
module TestModule;

// Inputs

reg a;

reg b;

// Outputs

wire [0:6]y;

// Instantiate the Unit Under Test (UUT)

gates uut (a,b,y);

initial begin

// Initialize Inputs

a = 0; b = 0;

// Wait 100 ns for global reset to finish

#1

a = 0;b = 1;

#1

a = 1;


b = 0;

#1

a = 1;
```

```
b = 1;  
  
end  
  
endmodule
```

Waveform

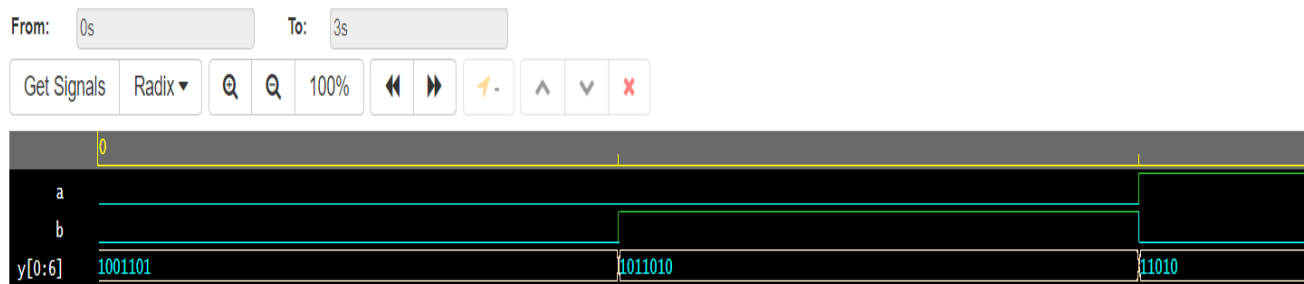

1 b

To design and develop Verilog HDL code to realize the given three variables and four variable functions.

$$(a,b,c) = \sum m(1,2,3,4,5,6)$$


Solution:

$$\text{Minterm} = \sum m(1, 2, 3, 4, 5, 6)$$

Variable = 3

As Max of Minterm is 6, So we have taken N = 3
and Variable = a,b,c

a\b,c	00	01	11	10
0	0	1	1	1
1	1	1	0	1

 

Code

```

Dataflow Modelling
module exp(a,b,c,y);
input a,b,c;
output y;
assign y = ( b & ~c) | (~a & c)| (a & ~b);
endmodule

```

```

Behavioural Modelling
module exp(a,b,c,y);
input a,b,c;
output reg y;
always @(*)

begin

y = ( b & ~c) | (~a & c)| (a & ~b);
end
endmodule

```

```

Structural Modelling
module exp(a,b,c,y);
input a,b,c;
output y;
wire t1,t2,t3,u1,u2,u3;

not n1(t1,a);
not n2(t2,b);
not n3(t3,c);

and a1(u1,b,t3);
and a2(u2,t1,c);
and a3(u3,a,t2);

or o1(y,u1,u2,u3);
endmodule

```

Test bench

```

module ex_tb;
wire y;
reg a,b,c;

exp a1(a,b,c,y);

initial begin
a=0; b=0; c=0;
a=0; b=0; c=1;
a=0; b=1; c=0;
a=0; b=1; c=1;
a=1; b=0; c=0;
a=1; b=0; c=1;
a=1; b=1; c=0;
a=1; b=1; c=1;
end

endmodule

```

2. $f(a,b,c,d) = \sum m(0,1,4,8,9,10)$


Solution:

$$\text{Minterm} = \sum m(0, 1, 4, 8, 9, 10)$$

Variable = 4

As Max of Minterm is 10, So we have taken $N = 4$
and Variable = a,b,c,d

a,b \ c,d	00	01	11	10
00	1 <small>0</small>	1 <small>1</small>	0 <small>3</small>	0 <small>2</small>
01	1 <small>4</small>	0 <small>5</small>	0 <small>7</small>	0 <small>6</small>
11	0 <small>12</small>	0 <small>13</small>	0 <small>15</small>	0 <small>14</small>
10	1 <small>8</small>	1 <small>9</small>	0 <small>11</small>	1 <small>10</small>

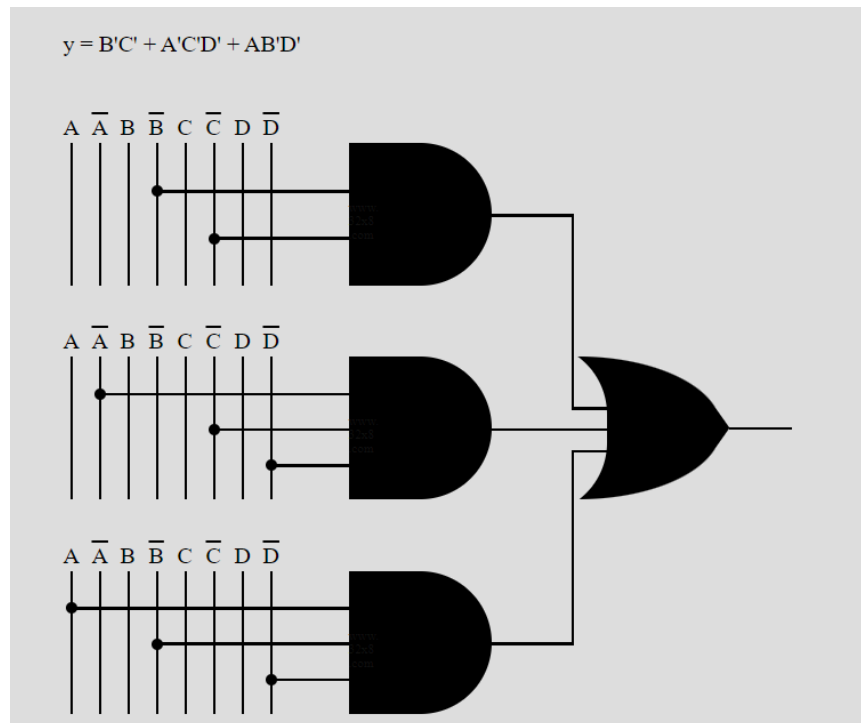

Code

Dataflow Modelling

```
module exp(a,b,c,d,y);  
input a,b,c,d;  
output y;  
assign y = ( ~b & ~c) | (~a & ~c& ~d)| (a & ~b &~d);  
endmodule
```

Behavioural Modelling

```
module exp(a,b,c,d,y);  
input a,b,c,d;  
output reg y;  
always @(*)  
  
begin  
  
y = ( ~b & ~c) | (~a & ~c& ~d)| (a & ~b &~d);  
end  
endmodule
```

Structural Modelling

```
module exp(a,b,c,d,y);  
input a,b,c,d;  
output y;  
wire t1,t2,t3,t4,u1,u2,u3;  
  
not n1(t1,a);  
not n2(t2,b);  
not n3(t3,c);  
not n4(t4,d);  
  
and a1(u1,t2,t3);  
and a2(u2,t1,t3,t4);  
and a3(u3,a,t2,t4);  
  
or o1(y,u1,u2,u3);  
endmodule
```

Test Bench

```
module ex_tb;
wire y;
reg a,b,c,d;

exp a1(a,b,c,d,y);

initial begin
a=0; b=0; c=0; d=0;
a=0; b=0; c=0; d=1;
a=0; b=0; c=1; d=0;
a=0; b=0; c=1; d=1;
a=0; b=1; c=0; d=0;
a=0; b=1; c=0; d=1;
a=0; b=1; c=1; d=0;
a=0; b=1; c=1; d=1;
a=1; b=0; c=0; d=0;
a=1; b=0; c=0; d=1;
a=1; b=0; c=1; d=0;
a=1; b=0; c=1; d=1;
a=1; b=1; c=0; d=0;
a=1; b=1; c=0; d=1;
a=1; b=1; c=1; d=0;
a=1; b=1; c=1; d=1;
end


endmodule
```

Experiment -2

Aim : To design and develop Verilog HDL code and implement for the following combinational circuits .

Decoder

Block Diagram:

 

Truth Table:

Enable	INPUTS			Outputs							
E	A ₂	A ₁	A ₀	Y ₇	Y ₆	Y ₅	Y ₄	Y ₃	Y ₂	Y ₁	Y ₀
0	x	x	x	0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	1
1	0	0	1	0	0	0	0	0	0	1	0
1	0	1	0	0	0	0	0	0	1	0	0
1	0	1	1	0	0	0	0	1	0	0	0
1	1	0	0	0	0	0	1	0	0	0	0
1	1	0	1	0	0	1	0	0	0	0	0
1	1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	1	0	0	0	0	0	0	0

The logical expression of the term Y₀, Y₁, Y₂, Y₃, Y₄, Y₅, Y₆, and Y₇ is as follows:

$$Y_0 = A_0' \cdot A_1' \cdot A_2'$$

$$Y_1 = A_0 \cdot A_1' \cdot A_2'$$

$$Y_2 = A_0' \cdot A_1 \cdot A_2'$$

$$Y_3 = A_0 \cdot A_1 \cdot A_2'$$

$$Y_4 = A_0' \cdot A_1' \cdot A_2$$

$$Y_5 = A_0 \cdot A_1' \cdot A_2$$

$$Y_6 = A_0' \cdot A_1 \cdot A_2$$

$$Y_7 = A_0 \cdot A_1 \cdot A_2$$

//declare the Verilog module - The inputs and output port names.

```
module decoder3to8(Data_in,en,Data_out);
```

```
    //what are the input ports and their sizes.
```

```
    input [2:0] Data_in;
```

```
    input en;
```

```
    //what are the output ports and their sizes.
```

```

output [7:0] Data_out;

//Internal variables
reg [7:0] Data_out;

//Whenever there is a change in the Data_in, execute the always block.
always @(Data_in or en)
begin
if(en==0)
begin
Data_out=8'b0;
end
else
begin
case (Data_in) //case statement. Check all the 8 combinations.
3'b000 : Data_out = 8'b00000001;
3'b001 : Data_out = 8'b00000010;
3'b010 : Data_out = 8'b00000100;
3'b011 : Data_out = 8'b00001000;
3'b100 : Data_out = 8'b00010000;
3'b101 : Data_out = 8'b00100000;
3'b110 : Data_out = 8'b01000000;
3'b111 : Data_out = 8'b10000000;

//To make sure that latches are not created create a default value for output.
default : Data_out = 8'b00000000;

endcase
end
endmodule

```

Testbench

```
module tb_decoder;

    // Declaring Inputs
    reg [2:0] Data_in;
    reg en;

    // Declaring Outputs
    wire [7:0] Data_out;

    // Instantiate the Unit Under Test (UUT)
    decoder3to8 uut (.Data_in(Data_in), .en(en), .Data_out(Data_out));

    initial begin
        #100 en=1'b0;
        #100 en=1'b1;

        Data_in = 3'b000;    #100;
        Data_in = 3'b001;    #100;
        Data_in = 3'b010;    #100;
        Data_in = 3'b011;    #100;
        Data_in = 3'b100;    #100;
        Data_in = 3'b101;    #100;
        Data_in = 3'b110;    #100;
        Data_in = 3'b111;    #100;

        end
```

endmodule

8 : 3 Encoder (Octal to Binary) –

The 8 to 3 Encoder or octal to Binary encoder consists of **8 inputs** : Y7 to Y0 and **3 outputs** : A2, A1 & A0. Each input line corresponds to each octal digit and three outputs generate corresponding binary code.

The figure below shows the logic symbol of octal to binary encoder:

Inputs								Outputs			
A7	A6	A5	A4	A3	A2	A1	A0	Y2	Y1	Y0	Valid
0	0	0	0	0	0	0	0	X	X	X	0
0	0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	0	1	X	0	0	1	1
0	0	0	0	0	1	X	X	0	1	0	1
0	0	0	0	1	X	X	X	0	1	1	1
0	0	0	1	X	X	X	X	1	0	0	1
0	0	1	X	X	X	X	X	1	0	1	1
0	1	X	X	X	X	X	X	1	1	0	1
1	X	X	X	X	X	X	X	1	1	1	1

Verilog code

// Code your design here

```
module encoder8_3(en, a_in, y_op,v);
```

```
input en;
```

```
input [7:0] a_in;
```

```
output reg v;
```

```
output [2:0] y_op;
```

```
reg [2:0] y_op;
```

```
always @ (a_in,en)
```

```
begin
```

```

if(en==0 )

    begin

        y_op =3'bxxx;

        v=1'b0;

    end

else

    begin

        v=1'b1;

    case (a_in)

8'b00000001: y_op = 3'b000;

8'b00000010: y_op = 3'b001;

8'b00000100: y_op = 3'b010;

8'b00001000: y_op = 3'b011;

8'b00010000: y_op = 3'b100;

8'b00100000: y_op = 3'b101;

8'b01000000: y_op = 3'b110;

8'b10000000: y_op = 3'b111;

default: y_op =3'bzzz;

    endcase

end

end

endmodule

```

Test bench

// Code your testbench here

// or browse Examples


```

module encodertest_tb;

// Inputs

reg en;

reg [7:0] a_in;


// Outputs

wire v;

wire [2:0] y_op;


// Instantiate the Unit Under Test (UUT)

encoder8_3 uut(en,a_in,y_op,v);


initial begin

    $dumpfile("dump.vcd");

    $dumpvars(1);

    a_in = 8'b00000000;

    en = 1'b0;


    #10 en = 1'b1; a_in = 8'b00000001;

    #10 a_in = 8'b00000010;

    #10 a_in = 8'b00000100;

    #10 a_in = 8'b00001000;

    #10 a_in = 8'b00010000;

    #10 a_in = 8'b00100000;


```

```
#10 a_in = 8'b01000000;

#10 a_in = 8'b10000000;

end
```

```
endmodule
```

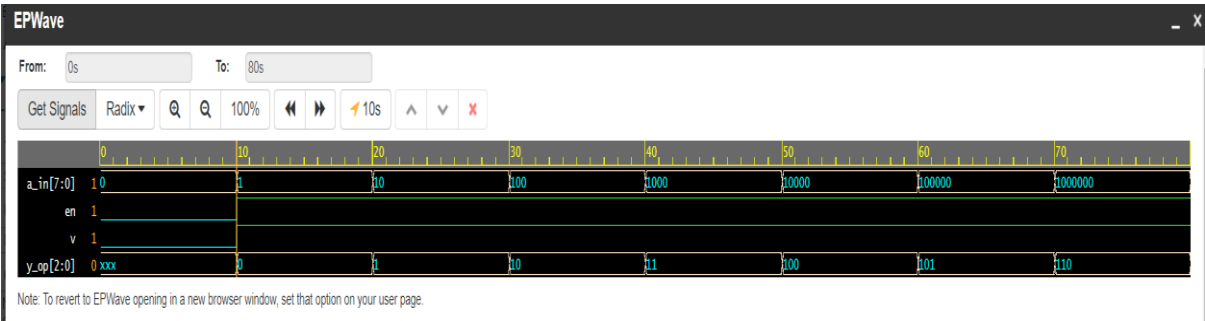

8 to 3 Priority Encoder

This kind of encoder is also named an 8-bit or Octal to Binary priority encoder. This type of encoder consists of 8 inputs and 3 outputs. When multiple inputs are active high at the same time, the input with the highest priority is considered to represent the output.

Inputs								Outputs			
A7	A6	A5	A4	A3	A2	A1	A0	Y2	Y1	Y0	Valid
0	0	0	0	0	0	0	0	X	X	X	0
0	0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	0	1	X	0	0	1	1
0	0	0	0	0	1	X	X	0	1	0	1
0	0	0	0	1	X	X	X	0	1	1	1
0	0	0	1	X	X	X	X	1	0	0	1
0	0	1	X	X	X	X	X	1	0	1	1
0	1	X	X	X	X	X	X	1	1	0	1
1	X	X	X	X	X	X	X	1	1	1	1

```
module prio_enco(en, a_in, y_op,v);

input en;
```

```
input [7:0] a_in;

output reg v;

output [2:0] y_op;

reg [2:0] y_op;

always @ (a_in,en)

begin

    if(en==0 )

        begin

            y_op =3'bxxx;

            v=1'b0;

        end

    else

        begin

            v=1'b1;

        case (a_in)

            8'b00000001: y_op =3'b000;

            8'b0000001x: y_op= 3'b001;

            8'b000001xx: y_op= 3'b010;

            8'b00001xxx: y_op= 3'b011;

            8'b0001xxxx: y_op= 3'b100;

            8'b001xxxxx: y_op= 3'b101;

            8'b01xxxxxx: y_op= 3'b110;

            8'b1xxxxxxx: y_op= 3'b111;

            default: y_op=3'bzzz;

        endcase

    end
```

```
end
```

```
end
```

```
endmodule
```

Test bench

```
// Code your testbench here
```

```
// or browse Examples
```

```
module encoder_prio_test_tb;
```

```
// Inputs
```

```
reg en;
```

```
reg [7:0] a_in;
```

```
// Outputs
```

```
wire v;
```

```
wire [2:0] y_op;
```

```
// Instantiate the Unit Under Test (UUT)
```

```
prio_enco uut(en,a_in,y_op,v);
```

```
initial begin
```

```
    $dumpfile("dump.vcd");
```

```
    $dumpvars(1);
```

```
a_in = 8'b00000000;
```

```
en = 1'b0;
```

```
#10 en = 1'b1; a_in = 8'b000000001;
```

```
#10 a_in = 8'b000000010;
```

```
#10 a_in = 8'b000000100;
```

```
#10 a_in = 8'b000001000;
```

```
#10 a_in = 8'b000010000;
```

```
#10 a_in = 8'b000100000;
```


```
#10 a_in = 8'b001000000;
```

```
#10 a_in = 8'b010000000;
```

```
end
```

```
endmodule
```


3. 8 : 1 mux using 4:1 mux and 2:1 mux

 


8 :1 Mux

Inputs			Output
S_2	S_1	S_0	O
0	0	0	I_0
0	0	1	I_1
0	1	0	I_2
0	1	1	I_3
1	0	0	I_4
1	0	1	I_5
1	1	0	I_6
1	1	1	I_7

8:1 mux using 4:1 and 2:1

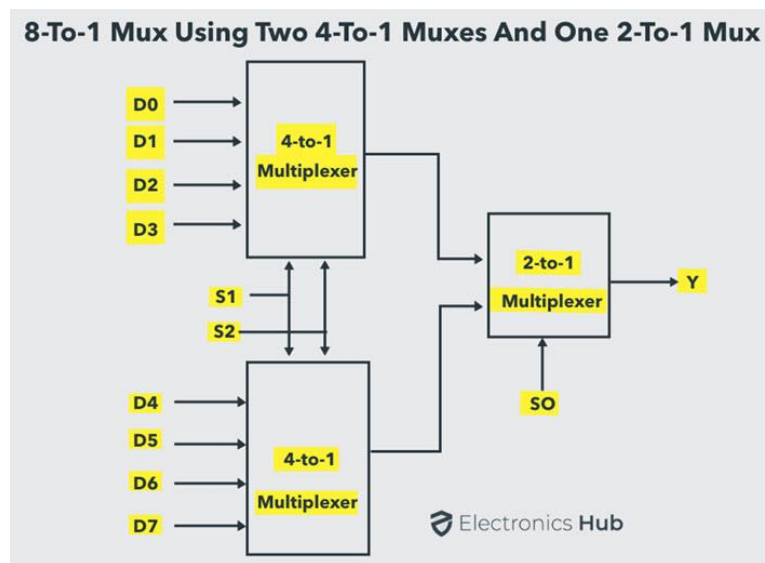

 

```
// Code your design here
module mux2to1(a,b,sel,out);
    input a,b,sel;
    output out;
    bufif1 (out,a,sel);
    bufif0 (out,b,sel);
endmodule

module mux4to1(a,sel,out);
    input [3:0] a;
    input [1:0] sel;
    output out;
    wire mux_1,mux_2;
    mux2to1 m1 (a[3],a[2],sel[0],mux_1);
    mux2to1 m2 (a[1],a[0],sel[0],mux_2);
    mux2to1 m3 (mux_1,mux_2,sel[1],out);
endmodule

module mux8to1(a,sel,out);
    input [7:0] a;
    input [2:0] sel;
    output out;

    wire mux_1,mux_2;

    mux4to1 m1 (a[7:4],sel[1:0],mux_1),
              m2 (a[3:0],sel[1:0],mux_2);
    mux2to1 m3 (mux_1,mux_2,sel[2],out);
endmodule
```

```

// Code your testbench here
// or browse Examples
// Code your testbench here
// or browse Examples
module TB_MUX_8;
reg [7:0] d;
reg [2:0] sel;
wire out;

// Basic Gates is what we are going to test.
mux8to1 U1(d,sel,out);

initial
begin
$dumpvars(1);
    d[0] = 1;
    d[1] = 1;
    d[2] = 1;
    d[3] = 1;
    d[4] = 1;
    d[5] = 0;
    d[6] = 0;
    d[7] = 0;
    sel[2] = 1;
    sel[1] = 0;
    sel[0] = 0;

#1
    d[0] = 0;
    d[1] = 0;
    d[2] = 0;
    d[3] = 0;
    d[4] = 0;
    d[5] = 1;
    d[6] = 1;
    d[7] = 1;
    sel[2] = 1;
    sel[1] = 1;
    sel[0] = 0;

```

```

#1
d[0] = 0;
d[1] = 0;
d[2] = 0;
d[3] = 0;
d[4] = 1;
d[5] = 0;
d[6] = 1;
d[7] = 0;
sel[2] = 1;
sel[1] = 1;
sel[0] = 1;

end
endmodule


```


4) 4- bit Binary to Gray Code Converter

Using Exclusive-Or (\oplus) operation –

This is very simple method to get Gray code from Binary number. These are following steps for n -bit binary numbers –

 - The most significant bit (MSB) of the Gray code is always equal to the MSB of the given Binary code.
- Other bits of the output Gray code can be obtained by XORing binary code bit at the index and previous index.




Gray to binary

Using Exclusive-Or (\oplus) operation –

This is very simple method to get Binary number from Gray code. These are following steps for n -bit binary numbers –

 - The Most Significant Bit (MSB) of the binary code is always equal to the MSB of the given binary number.
- Other bits of the output binary code can be obtained by checking gray code bit at that index. If current gray code bit is 0, then copy previous binary code bit, else copy invert of previous binary code bit.



The truth table for the conversion is-

BINARY INPUT				GRAY CODE OUTPUT			
B3	B2	B1	B0	G3	G2	G1	G0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	0
0	1	0	1	0	1	1	1
0	1	1	0	0	1	0	1
0	1	1	1	0	1	0	0
1	0	0	0	1	1	0	0
1	0	0	1	1	1	0	1
1	0	1	0	1	1	1	1
1	0	1	1	1	1	1	0
1	1	0	0	1	0	1	0
1	1	0	1	1	0	1	1
1	1	1	0	1	0	0	1
1	1	1	1	1	0	0	0

K-Map Simplification

K – map for G₀:

		B1B0			
		00	01	11	10
B3B2	00	0	1	0	1
	01	0	1	0	1
	11	0	1	0	1
	10	0	1	0	1

$$\begin{aligned}
 G_0 &= B1B0 + B1B0 \\
 &= B1 \oplus B0
 \end{aligned}$$

K- map for G1:

		B1B0			
		00	01	11	10
B3B2	00	0	0	1	1
	01	1	1	0	0
	11	1	1	0	0
	10	0	0	1	1

$$G1 = \overline{B1}B2 + B1\overline{B2}$$

$$= B1 \oplus B2$$

K- map for G2:

		B1B0			
		00	01	11	10
B3B2	00	0	0	0	0
	01	0	0	0	0
	11	1	1	1	1
	10	1	1	1	1


$$G2 = \overline{B3}B2 + B3\overline{B2}$$

$$= B3 \oplus B2$$

K- map for G3:

		B1B0			
		00	01	11	10
B3B2	00	0	0	0	0
	01	1	1	1	1
	11	0	0	0	0
	10	1	1	1	1

$$G3 = B3$$

 

Data Flow

```

`timescale 1 ns/1 ns
module binary_gray (b,g);
input [3:0]b;
output [3:0]g;
assign g[0] =b[1] ^ b[0];
assign g[1] =b[2] ^ b[1];
assign g[2]=b[3] ^ b[2];
assign g[3] = b[3];
endmodule

```

Structural Style

```

`timescale 1ns/1ns
module binary_gray (b,g);
input [3:0]b;
output [3:0]g;
xor A1( g[0],b[1], b[0]);
xor A2( g[1],b[2], b[1]);
xor A3( g[2],b[3], b[2]);
buf A4( g[3] , b[3]);
endmodule

```


Behavioural Flow

```
`timescale 1ns/1ns
module binary_gray (b,g);
input [3:0]b;
output [3:0]g;
reg[3:0]g;
always@(b)
begin
g[0] =b[1] ^ b[0];
g[1] =b[2] ^ b[1];
g[2]=b[3] ^ b[2];
g[3] = b[3];
end
endmodule
```

Test Bench

```
`timescale 1ns/1ns
module binary_gray_tb;
reg [3:0]b;
wire [3:0]g;
binary_gray A1(.b(b) , .g(g));
initial
begin
b=4'b0000;
#100 b=4'b0001;
#100 b=4'b0010;
#100 b=4'b0011;
end
endmodule
```

Expected Waveform

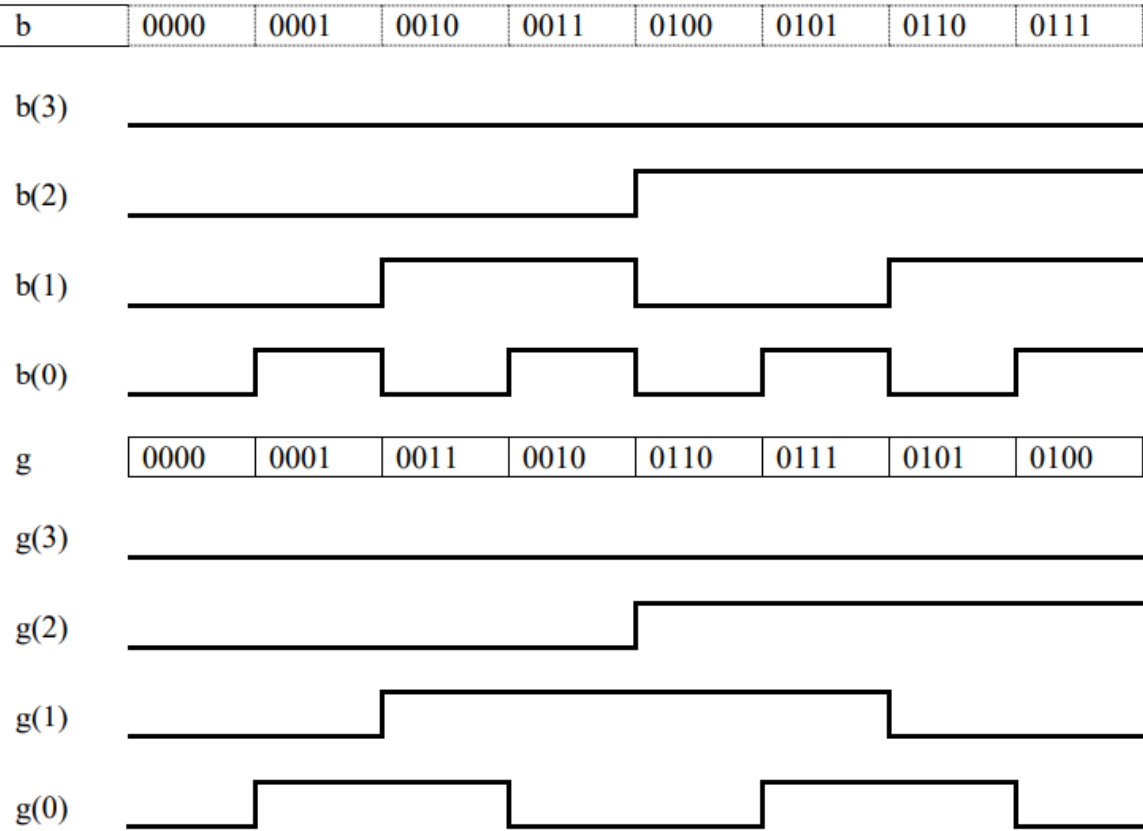

Binary to Gray

Gray Code Input				Binary Code Output			
G3	G2	G1	G0	B3	B2	B1	B0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	1	0	0	1	0
0	0	1	0	0	0	1	1
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	1
0	1	0	1	0	1	1	0
0	1	0	0	0	1	1	1
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	1
1	1	1	1	1	0	1	0
1	1	1	0	1	0	1	1
1	0	1	0	1	1	0	0
1	0	1	1	1	1	0	1
1	0	0	1	1	1	1	0
1	0	0	0	1	1	1	1

Table1

		G1G0			
G3G2		00	01	11	10
	00	0	0	0	0
	01	0	0	0	0
	11	1	1	1	1
	10	1	1	1	1

Fig6 (a): K – map for B_3

Simplified expression $B_3 = G_3$

For output B_2

		G1G0			
G3G2		00	01	11	10
	00	0	0	0	0
	01	1	1	1	1
	11	0	0	0	0
	10	1	1	1	1

Fig6 (b): K – map for B_2

$$B_2 = G_3(G_2) + G_2(G_3) = G_3 \oplus G_2$$

For output B_1

		G1G0			
G3G2		00	01	11	10
	00	0	0	1	1
	01	1	1	0	0
	11	0	0	1	1
	10	1	1	0	0

$$B_1 = G_3 \oplus G_2 \oplus G_1$$

Fig6 (c): K – map for B_1

$$\begin{aligned}
 B_1 &= G_1 \overline{G_2} \overline{G_3} + G_2 \overline{G_3} \overline{G_1} + G_3 G_2 G_1 + G_3 \overline{G_1} \overline{G_2} = \overline{G_1} (G_3 \oplus G_2) + G_1 (\overline{G_3} \oplus \overline{G_2}) \\
 &= \overline{G_1} X + G_1 \overline{X} \text{ where } X = G_3 \oplus G_2 \\
 &= G_1 \oplus X = G_1 \oplus G_2 \oplus G_3
 \end{aligned}$$

For output B_0

G3G2 \ G1G0	00		01		11		10	
	0	1	0	1	0	1	0	1
00	0	1	0	1	0	1	0	1
01	1	0	1	0	1	0	1	0
11	0	1	0	1	0	1	0	1
10	1	0	1	0	1	0	1	0

Fig6 (d): K – map for B_0

$$\begin{aligned}
 B_0 &= G_0 \overline{G_1} \overline{G_2} \overline{G_3} + G_2 \overline{G_3} \overline{G_1} \overline{G_0} + G_1 \overline{G_3} \overline{G_2} \overline{G_0} + G_1 \overline{G_3} \overline{G_2} \overline{G_0} + G_2 \overline{G_3} \overline{G_1} \overline{G_0} + G_2 \overline{G_1} \overline{G_3} \overline{G_0} \\
 &+ G_2 \overline{G_0} \overline{G_3} \overline{G_1} + G_3 \overline{G_1} \overline{G_2} \overline{G_0} + G_0 \overline{G_2} \overline{G_3} \overline{G_1} \\
 &= \overline{G_1} \overline{G_0} (G_3 \oplus G_2) + G_0 \overline{G_1} (\overline{G_3} \oplus \overline{G_2}) + G_0 \overline{G_1} (\overline{G_3} \oplus \overline{G_2}) + G_1 \overline{G_0} (\overline{G_3} \oplus \overline{G_2}) \\
 &= (G_3 \oplus G_2) + (\overline{G_1} \oplus \overline{G_0}) + (G_1 \oplus G_0) + (\overline{G_3} \oplus \overline{G_2}) \\
 &= \overline{Y} X + Y \overline{X} \text{ where } X = G_3 \oplus G_2 \text{ and } Y = G_1 \oplus G_0 \\
 &= (G_2 \oplus G_3) \oplus (G_1 \oplus G_0) \\
 &= G_2 \oplus G_3 \oplus G_1 \oplus G_0
 \end{aligned}$$

Step3: Realization

The Gray to Binary code converter is as shown in figure 7.

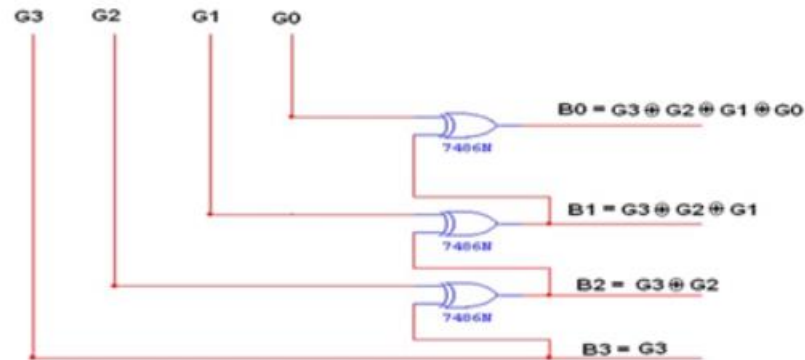


Fig7: Gray to binary code converter

Gate level Modelling

```
module gray_to_binary(g,b);
input [3:0]g;
output [3:0]b;
buf(b[3],g[3]);
xor x1 (b[2],g[2],g[3]);
xor x2(b[1],g[1],g[2],g[3]);
xor x3 (b[0],g[0],g[1],g[2],g[3]);
endmodule
```

Dataflow

```
module gray_to_binary(g,b);
input [3:0]g;
output [3:0]b;

assign b[3]=g[3];
assign b[2]=g[2]^g[3];
assign b[1]= g[1]^g[2]^g[3];
assign b[0]= g[0]^g[1]^g[2]^g[3];
endmodule
```

Behavioral Modelling

```
module gray_to_binary(g,b);
input [3:0]g;
output reg [3:0]b;

always @(g)
begin
  b[3]=g[3];
  b[2]=g[2]^g[3];
  b[1]= g[1]^g[2]^g[3];
  b[0]= g[0]^g[1]^g[2]^g[3];
end
endmodule
```

Testbench


```
module g_to_b_tb;
reg [3:0]g;
wire [3:0]b;

gray_to_binary uut(.g(g),.b(b));

initial begin

g= 4'b0000;
#10 g=4'b0001;
#10 g=4'b0011;
#10 g=4'b1111;
end
endmodule
```

5) 1: 8 Multiplexer

 

S2	S1	S0	O0	O1	O2	O3	O4	O5	O6	O7
0	0	0	I	0	0	0	0	0	0	0
0	0	1	0	I	0	0	0	0	0	0
0	1	0	0	0	I	0	0	0	0	0
0	1	1	0	0	0	I	0	0	0	0
1	0	0	0	0	0	0	I	0	0	0
1	0	1	0	0	0	0	0	I	0	0
1	1	0	0	0	0	0	0	0	I	0
1	1	1	0	0	0	0	0	0	0	I

Verilog Code :

```
module Demultiplexer(in,s0,s1,s2,d0,d1,d2,d3,d4,d5,d6,d7);
input in,s0,s1,s2;
output d0,d1,d2,d3,d4,d5,d6,d7;
assign d0=(in & ~s2 & ~s1 &~s0),
d1=(in & ~s2 & ~s1 &s0),
d2=(in & ~s2 & s1 &~s0),
d3=(in & ~s2 & s1 &s0),
d4=(in & s2 & ~s1 &~s0),
d5=(in & s2 & ~s1 &s0),
d6=(in & s2 & s1 &~s0),
d7=(in & s2 & s1 &s0);
endmodule
```

Test Bench

Test Bench

```
`timescale 1ns / 1ps
```

```
// Inputs
```

```
reg in;
```

```
reg s0;
```

```
reg s1;
```

```
reg s2;
```

```
// Outputs
```

```
wire d0;
```

```
wire d1;
```

```
wire d2;
```

```
wire d3;
```

```
wire d4;
```

```
wire d5;
```

```
wire d6;
```

```
wire d7;
```

```
// Instantiate the Unit Under Test (UUT)
```

```
Demultiplexer uut (
```

```
.in(in),
```

```
.s0(s0),
```

```
.s1(s1),
```

```
.s2(s2),
```

```
.d0(d0),
```

```
.d1(d1),
```

```
.d2(d2),
```

```
.d3(d3),
```

```
.d4(d4),
```

```
.d5(d5),
```

```
.d6(d6),
```

```
.d7(d7)
```

```
);
```

```
initial begin
```

```
// Initialize Inputs
```

```
in = 0;
```

```
s0 = 0;
```

```
s1 = 0;
```

```
s2 = 0;
```

```
// Wait 100 ns for global reset to finish
```

```
#100;
```

```
in = 1;
```

```
s0 = 0;
```

```
s1 = 1;
```

```
s2 = 0;
```

```
// Wait 100 ns for global reset to finish
```

```
#100;

// Add stimulus here

end

endmodule
```

6) 2 BIT COMPARATOR

Inputs				Outputs		
A ₁	A ₀	B ₁	B ₀	A>B	A=B	A<B
0	0	0	0	0	1	0
0	0	0	1	0	0	1
0	0	1	0	0	0	1
0	0	1	1	0	0	1
0	1	0	0	1	0	0
0	1	0	1	0	1	0
0	1	1	0	0	0	1
0	1	1	1	0	0	1
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	0	1	0
1	0	1	1	0	0	1
1	1	0	0	1	0	0
1	1	0	1	1	0	0
1	1	1	0	1	0	0
1	1	1	1	0	1	0

```
module comparator(input [1:0] A,B, output A_less_B,
A_equal_B, A_greater_B);
  wire tmp1,tmp2,tmp3,tmp4,tmp5, tmp6, tmp7, tmp8;
  // A = B output
  xnor u1(tmp1,A[1],B[1]);
  xnor u2(tmp2,A[0],B[0]);
  and u3(A_equal_B,tmp1,tmp2);
  // A less than B output
  assign tmp3 = (~A[0]) & (~A[1]) & B[0];
  assign tmp4 = (~A[1]) & B[1];
  assign tmp5 = (~A[0]) & B[1] & B[0];
  assign A_less_B = tmp3 | tmp4 | tmp5;
  // A greater than B output
```

```

assign tmp6 = (~B[0]) & (~B[1]) & A[0];
assign tmp7 = (~B[1]) & A[1];
assign tmp8 = (~B[0]) & A[1] & A[0];
assign A_greater_B = tmp6 | tmp7 | tmp8;
endmodule

`timescale      10 ps/ 10 ps
// FPGA projects using Verilog/ VHDL
// fpga4student.com
// Verilog testbench code for 2-bit comparator
module tb_comparator;
reg [1:0] A, B;
wire A_less_B, A_equal_B, A_greater_B;
integer i;
// device under test
comparator dut(A,B,A_less_B, A_equal_B, A_greater_B);
initial begin
    for (i=0;i<4;i=i+1)
    begin
        A = i;
        B = i + 1;
        #20;

    end
    for (i=0;i<4;i=i+1)
    begin
        A = i;
        B = i;
        #20;

    end
    for (i=0;i<4;i=i+1)
    begin
        A = i+1;
        B = i;
        #20;


    end
end
endmodule

```

Experiment 3

Write an HDL code to describe the functions of a Half Adder and full adder

Half Adder Truth Table			
A	B	Carry	Sum
0	0	0	0
1	0	0	1
0	1	0	1
1	1	1	0

 

Half-Adder Schematic - From Wikipedia

```
////////////////////////////////////  
// File Downloaded from http://www.nandland.com  
////////////////////////////////////  
module half_adder  
(  
    i_bit1,  
    i_bit2,  
    o_sum,  
    o_carry  
);  
  
input  i_bit1;  
input  i_bit2;  
output o_sum;  
output o_carry;  
  
assign o_sum  = i_bit1 ^ i_bit2; // bitwise xor  
assign o_carry = i_bit1 & i_bit2; // bitwise and  
  
endmodule // half_adder
```

Test bench

```
/ File Downloaded from http://www.nandland.com  
////////////////////////////////////  
`include "half_adder.v"  
  
module half_adder_tb;  
  
    reg r_BIT1 = 0;  
    reg r_BIT2 = 0;  
    wire w_SUM;  
  

```

```


wire w_CARRY;

half_adder half_adder_inst
(
    .i_bit1(r_BIT1),
    .i_bit2(r_BIT2),
    .o_sum(w_SUM),
    .o_carry(w_CARRY)
);

initial
begin
    r_BIT1 = 1'b0;
    r_BIT2 = 1'b0;
    #10;
    r_BIT1 = 1'b0;
    r_BIT2 = 1'b1;
    #10;
    r_BIT1 = 1'b1;
    r_BIT2 = 1'b0;
    #10;
    r_BIT1 = 1'b1;
    r_BIT2 = 1'b1;
    #10;
end

endmodule // half_adder_tb

```

 


Modelsim Simulation of Half Adder

Full adder using half adder

Full adder Truth table

A	B	C	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 A Full adder can be implemented using half adders as shown below:



The Verilog code can be written in structural modelling for the above circuit.

//declare the Full adder verilog module.

```
module full_adder(  
    Data_in_A, //input A  
    Data_in_B, //input B  
    Data_in_C, //input C  
    Data_out_Sum,  
    Data_out_Carry  
);  
  
    //what are the input ports.  
    input Data_in_A;  
    input Data_in_B;  
    input Data_in_C;  
    //What are the output ports.  
    output Data_out_Sum;  
    output Data_out_Carry;  
    //Internal variables  
    wire ha1_sum;  
    wire ha2_sum;  
    wire ha1_carry;  
    wire ha2_carry;  
    wire Data_out_Sum;  
    wire Data_out_Carry;  
  
    //Instantiate the half adder 1  
    half_adder ha1(  
        .Data_in_A(Data_in_A),  
        .Data_in_B(Data_in_B),  
        .Data_out_Sum(ha1_sum),  
        .Data_out_Carry(ha1_carry)
```

```

);

//Instantiate the half adder 2
half_adder ha2(
    .Data_in_A(Data_in_C),
    .Data_in_B(ha1_sum),
    .Data_out_Sum(ha2_sum),
    .Data_out_Carry(ha2_carry)
);

//sum output from 2nd half adder is connected to full adder output
assign Data_out_Sum = ha2_sum;
//The carry's from both the half adders are OR'ed to get the final
carry./
assign Data_out_Carry = ha1_carry | ha2_carry;

endmodule

```

Testbench Code for Full Adder:

```

module tb_fullAdd;

    // Inputs
    reg Data_in_A;
    reg Data_in_B;
    reg Data_in_C;

    // Outputs
    wire Data_out_Sum;
    wire Data_out_Carry;

    // Instantiate the Unit Under Test (UUT)
    full_adder uut (
        .Data_in_A(Data_in_A),
        .Data_in_B(Data_in_B),
        .Data_in_C(Data_in_C),
        .Data_out_Sum(Data_out_Sum),
        .Data_out_Carry(Data_out_Carry)
    );

    initial begin
        //Apply inputs. 8 combinations of inputs are possible.
        //They are given below.
        Data_in_A = 0; Data_in_B = 0; Data_in_C = 0; #100;
        Data_in_A = 0; Data_in_B = 0; Data_in_C = 1; #100;
        Data_in_A = 0; Data_in_B = 1; Data_in_C = 0; #100;
        Data_in_A = 0; Data_in_B = 1; Data_in_C = 1; #100;
        Data_in_A = 1; Data_in_B = 0; Data_in_C = 0; #100;
        Data_in_A = 1; Data_in_B = 0; Data_in_C = 1; #100;
        Data_in_A = 1; Data_in_B = 1; Data_in_C = 0; #100;
        Data_in_A = 1; Data_in_B = 1; Data_in_C = 1; #100;
    end

endmodule

```


Simulated Waveform:

The code was synthesised and simulated in Xilinx ISE 13.1. The waveform is shown below:



Experiment 4

 Write a model for n bit ALU using the schematic diagram shown below



AIM: To design a verilog HDL for designing ALU using behavioral model. TOP MODULE

```
`timescale 1ns/1ns
module alu_32(en,opcode,a,b,y);
```

```
input en;
input [31:0]a,b; input
[2:0]opcode; output reg
[32:0]y;always@(*)
begin if(en==0)
y=33'bz; else
begin
case (opcode)
3'b000:y=a+b;
3'b001:y=a/b;

3'b010:y=a&b;
3'b011:y=a+b;

3'b100:y=a-b;

3'b101:y=a*b;
3'b110:y=a^b;
3'b111:y=`a;

endcase
```

```
endmodule
```

Experiment 5

Develop the HDL Code for the following flip-flops: SR, D, JK, and T

5. AIM: To design a Verilog HDL for designing J-K flip flop.

6. TOP MODULE

7.

8. `timescale 1ns/1ns

9. module jkff(j,k,clk,rst,q,nq);

10. input j,k,clk,rst;

11. output reg q,nq;

12. always @(posedge clk,rst) begin

13. if(reset)

14. q=1'b0;

15. else

16. begin

17. case({j,k})

18. 2'b00: begin q=q;

19. 2'b01: begin q=0;

20. 2'b10: begin q=1;

21. 2'b11: begin q=~q;

22. end

23. endcase

24. nq=~q;

25. end

26. endmodule

27.

28. TEST

BENCH29.

30. `timescale 1ns/1ns

31. module jkff_tb;

32. reg j,k,clk,rst;

33. wire q,nq;

34. jkff uut(.j(j),.k(k),.clk(clk),.rst(rst),.q(q),.nq(nq));

35. initial begin

36. rst=1;

37. j=0;k=0;

38. #100 rst=0;

39. #100 k=1;

40. #100 j=1;k=0;

41. #100 k=1;

42. end

43. endmodule

for SR FF 2'b11;q=1'bz; rest all is same. change the input and output variables name as SR. rest all same

AIM:To design a verilog HDL for designing t-flip flop

TOP MODULE

```
`timescale 1ns/1ns
module tff(t,clk,rst,q,nq);input
t,clk,rst,;
output reg q,nq; always
@(posedge clk)begin
if(rst)
q=1'b0;
else begin
case(t)
1'b0:q=0;
1'b1:q=~q;
endcase end
endmodule
```

TEST BENCH

```
`timescale 1ns/1nsmodule
tff_tb;
reg t,clk,rst;wire
q,nq;
tff uut(.t(t), .clk(clk) .rst(rst),.q(q),.nq(nq));initial begin
rst=1;
#100 rst=0:t=0;
#100 rst=0;t=1;
end endmodule
```


For D FF 1'b1:q=1; rest all same

Experiment 6

Synchronous and Asynchronous counterSynchronous BCD

(Decade)Counter

 A synchronous decade counter will count from zero to nine and repeat the sequence. The state diagram of this counter is shown in Fig



J	K	Q	Q+
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

Q	Q+	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

Characteristic Table

Present State				Next State				Output							
Q ₃	Q ₂	Q ₁	Q ₀	Q ₃	Q ₂	Q ₁	Q ₀	J ₃	K ₃	J ₂	K ₂	J ₁	K ₁	J ₀	K ₀
0	0	0	0	0	0	0	1	0	X	0	X	0	X	1	X
0	0	0	1	0	0	1	0	0	X	0	X	1	X	X	1
0	0	1	0	0	0	1	1	0	X	0	X	X	0	1	X
0	0	1	1	0	1	0	0	0	X	1	X	X	1	X	1
0	1	0	0	0	1	0	1	0	X	X	0	0	X	1	X
0	1	0	1	0	1	1	0	0	X	X	0	1	X	X	1
0	1	1	0	0	1	1	1	0	X	X	0	X	0	1	X
0	1	1	1	1	0	0	0	1	X	X	1	X	1	X	1
1	0	0	0	1	0	0	1	X	0	0	X	0	X	1	X
1	0	0	1	0	0	0	0	X	1	0	X	0	X	X	1

Q_1Q_0	00	01	11	10
Q_2Q_0	1	X	X	1
01	1	X	X	1
11	X	X	X	X
10	1	X	X	X

$J_0 = 1$

Q_1Q_0	00	01	11	10
Q_2Q_0	X	1	1	X
01	X	1	1	X
11	X	X	X	X
10	X	1	X	X

$K_0 = 1$

Q_1Q_0	00	01	11	10
Q_2Q_0		1	X	X
01		1	X	X
11	X	X	X	X
10			X	X

$J_1 = \bar{Q}_3 Q_0$

Q_1Q_0	00	01	11	10
Q_2Q_0	X	X	1	
01	X	X	1	
11	X	X	X	X
10	X	X	X	X

$K_1 = \bar{Q}_3 Q_0$

Q_1Q_0	00	01	11	10
Q_2Q_0			1	
01	X	X	X	X
11	X	X	X	X
10			X	X

$J_2 = Q_1 Q_0$

Q_1Q_0	00	01	11	10
Q_2Q_0	X	X	X	X
01			1	
11	X	X	X	X
10			X	X


$K_2 = Q_1 Q_0$

Q_1Q_0	00	01	11	10
Q_2Q_0				
01			1	
11	X	X	X	X
10	X	X	X	X

$J_3 = Q_3 Q_0 + Q_2 Q_1 Q_0$

Q_1Q_0	00	01	11	10
Q_2Q_0	X	X	X	X
01	X	X	X	X
11	X	X	X	X
10		1	X	X

$K_3 = Q_3 Q_0 + Q_2 Q_1 Q_0$

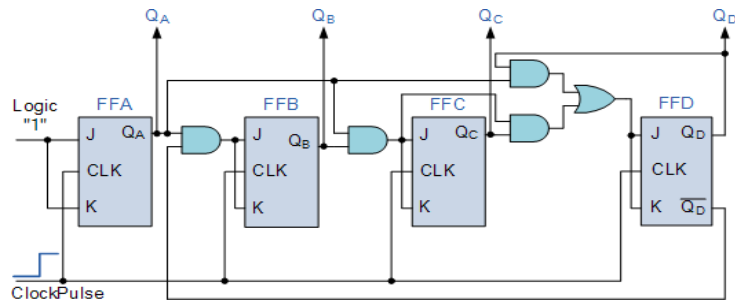


```

module jkfflop(input J, K , clk ,rst, output reg Q);
  always @(negedge clk) begin
    if(rst)
      Q <= 1'b0;
    else begin
      case({J,K})
        2'b00 : Q <= Q ;
        2'b01 : Q <= 1'b0;
        2'b10 : Q <= 1'b1;
        2'b11 : Q <= ~Q ;
      endcase
    end
  end
endmodule

```

```

module BCD_Counter(input clk, rst, output [3:0] Q);
  jkfflop first(1'b1 , 1'b1, clk ,rst, Q[0]);
  jkfflop second(~Q[3],~Q[3],Q[0],rst, Q[1]);
  jkfflop third(1'b1 , 1'b1 , Q[1] ,rst,Q[2]);
  jkfflop fourth(Q[1]&Q[2] , Q[3] , Q[0] ,rst, Q[3]);
endmodule

```

```


module TB;
  reg CLK = 0, rst = 1;
  wire[3:0] Q;
  BCD_Counter UUT(CLK ,rst, Q);

  initial repeat(40) #50 CLK=~CLK;
  initial #70 rst = 0;
endmodule

```

4-bit Asynchronous up counter using JK-FF (Structural model)

 Circuit Diagram for 4-bit Asynchronous up counter using JK-FF:



4-bit Asynchronous up counter using JK-FF (Structural model):

```
module async_count(j,k,clock,reset,q,qb);
input j,k,clock,reset;
output wire [3:0]q,qb;

jkff JK1(j,k,clock,reset,q[0],qb[0]);
jkff JK2(j,k,q[0],reset,q[1],qb[1]);
jkff JK3(j,k,q[1],reset,q[2],qb[2]);
jkff JK4(j,k,q[2],reset,q[3],qb[3]);

endmodule
```

Test bench

```
module async_tb;

reg j,k,clock,reset;

wire [3:0]q,qb;

async_count uut (j,k,clock,reset,q,qb);

initial begin

reset=1;

#10 reset=0;
```

```
j=4'b1111;
```

```
k=4'b1111;
```

```
end
```

```
endmodule
```